

# Circuit Analysis - Resistances, Voltage and Current Sources

Integrated Master Engineering Physics , Técnico, University of Lisbon

Laboratory Report 1

March 23, 2021

## Contents

<b>1</b>	<b>Introduction</b>	<b>1</b>
<b>2</b>	<b>Theoretical Analysis</b>	<b>2</b>
2.1	Mesh Method . . . . .	2
2.2	Nodal Method . . . . .	2
2.3	Comparing both methods . . . . .	3
<b>3</b>	<b>Simulation Analysis</b>	<b>3</b>
<b>4</b>	<b>Conclusion</b>	<b>3</b>

## 1 Introduction

The aim of this laboratory assignment is to study a circuit composed exclusively by voltage sources ( $V_a$  and  $V_c$ ), current sources ( $I_b$  and  $I_d$ ), as well as resistors ( $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ ,  $R_5$ ,  $R_6$  and  $R_7$ ). That being said, this circuit, which is shown in the image below, contains only linear components.

It was known beforehand that:  $R_1 = 1039.3 \, \Omega$ ,  $R_2 = 2010.9 \, \Omega$ ,  $R_3 = 30411.2 \, \Omega$ ,  $R_4 = 4183.8 \, \Omega$ ,  $R_5 = 3095.8 \, \Omega$ ,  $R_6 = 2021.2 \, \Omega$ ,  $R_7 = 1022.3 \, \Omega$ ,  $V_a = 5.1798 \, V$ ,  $I_d = 0.0010044 \, A$ ,  $K_b = 0.0070875 \, A/V$  and  $K_c = 8185.8 \, V/A$ .

Therefore, the objective was to find the values of:  $V_0$ ,  $V_1$ ,  $V_2$ ,  $V_3$ ,  $V_4$ ,  $V_5$ ,  $V_6$ ,  $V_7$ ,  $I_b$ ,  $I_c$ ,  $I_1$ ,  $I_2$ ,  $I_3$ ,  $I_4$ ,  $V_b$  and  $V_c$ .

In order to make it easier to analyse the circuit, both meshes and nodes were labelled.  $N_0$  was chosen as the ground node,  $V_0 = 0 \, V$ .  $V_i$  is the voltage in node  $N_i$  and  $I_1$  is the current that goes through mesh  $A$  counterclockwise. Likewise,  $I_2$  goes through  $B$ ,  $I_3$  through  $C$  and  $I_4$  through  $D$ , all anticlockwise. Besides that, in each resistance the direction of the current was arbitrarily chosen.

In Section 2, a theoretical analysis of the circuit is presented following two of the most common methods: the mesh method and the nodal method. In Section 3, the circuit is analysed by simulation. Finally, the comparison between both types of analysis and the conclusions of this study are in Section 4.

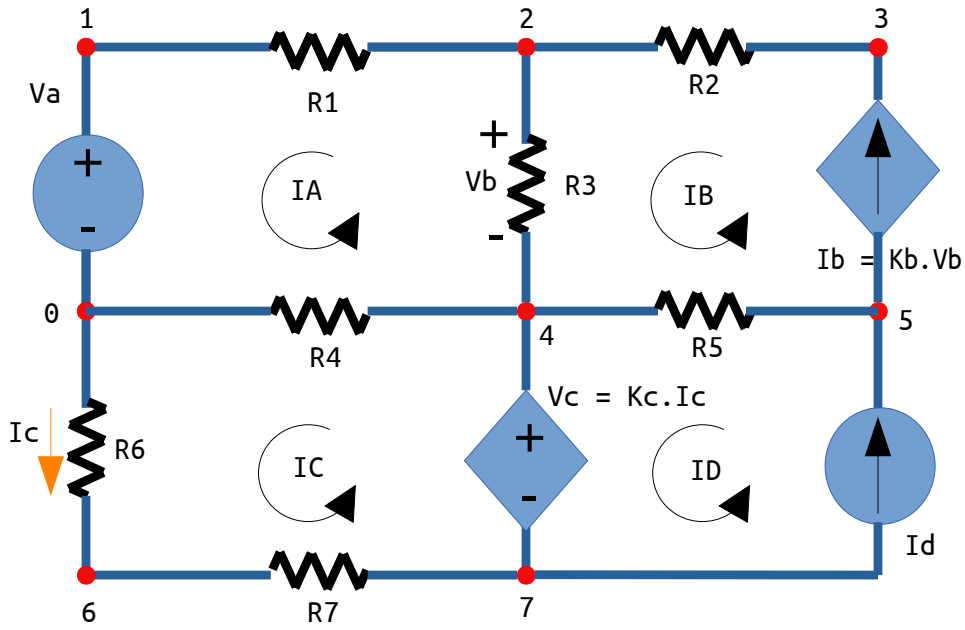


Figure 1: The circuit in study

## 2 Theoretical Analysis

### 2.1 Mesh Method

In the mesh method, equations are written for essential meshes, using Kirchhoff's voltage law (KVL), which states that "the directed sum of the potential differences (voltages) around any closed loop is zero". There are also additional equations.

In this method, as well as in the next one, Ohm's Law,  $V = RI \Leftrightarrow I = \frac{V}{R}$ , was used several times.

$$\begin{cases}
 R_6 I_3 + R_7 I_3 - V_c + R_4 (I_3 - I_1) = 0 & (1) \\
 V_a - R_4 (I_3 - I_1) - V_b + R_1 I_1 = 0 & (2) \\
 V_c = K_c I_c & (3) \\
 I_b = K_b V_b & (4) \\
 I_3 = I_c & (5) \\
 I_4 = I_d & (6) \\
 I_2 = I_b & (7) \\
 (I_2 - I_1) R_3 = V_b & (8)
 \end{cases} \quad (1)$$

### 2.2 Nodal Method

In the nodal method, a set of equation is written based on Kirchhoff's current law (KCL), according to which "the algebraic sum of currents in a network of conductors meeting at a point is zero", which means that the sum of currents flowing into that node is equal to the sum of currents flowing out of that node. Plus, there are some additional equations.

Name	Value [A or V]
$I_A$	-0.000067
$I_B$	0.025635
$I_C$	0.001189
$I_D$	0.001004

Table 1: Operating point. A variable preceded by @ is of type *current* and expressed in Ampere; other variables are of type *voltage* and expressed in Volt.

$$\begin{cases}
 V_0 = 0 & (1) \\
 V_1 - V_0 = V_a & (2) \\
 \frac{V_2 - V_1}{R_1} + \frac{V_2 - V_4}{R_3} + \frac{V_3 - V_2}{R_2} = 0 & (3) \\
 \frac{V_3 - V_2}{R_2} - (V_2 - V_4)K_b = 0 & (4) \\
 \frac{V_0 - V_6}{R_6} - \frac{V_6 - V_7}{R_7} = 0 & (5) \\
 \frac{V_5 - V_4}{R_5} + K_b(V_2 - V_4) - I_d = 0 & (6) \\
 V_4 - V_7 = K_c \frac{V_0 - V_6}{R_6} & (7) \\
 \frac{V_2 - V_4}{R_3} + \frac{V_5 - V_4}{R_5} + \frac{V_6 - V_7}{R_7} - \frac{V_4 - V_0}{R_4} - I_d = 0 & (8)
 \end{cases} \quad (2)$$

Name	Value [A or V]
$V_0$	0.000000
$V_1$	5.179800
$V_2$	4.949130
$V_3$	4.481100
$V_4$	4.981968
$V_5$	8.811951
$V_6$	-1.958148
$V_7$	-2.948538

Table 2: Operating point. A variable preceded by @ is of type *current* and expressed in Ampere; other variables are of type *voltage* and expressed in Volt.

**maybe explaining these equations a little better??**

## 2.3 Comparing both methods

After solving a linear system of equations with Octave, it was found out that.

## 3 Simulation Analysis

The aforementioned circuit was simulated using the ngspice simulator, which returned the following values:

## 4 Conclusion

In the end, one can say that the objectives defined for this laboratory session were met. The theoretical analysis, featuring both mesh and nodal methods, in which Octave maths tool was used, had results that proved to be consistent and coherent. As for the circuit simulation part with Ngspice, it was also well succeeded.

Name	Value [A or V]
@gb[i]	-2.32745e-04
@id[current]	1.004395e-03
@r1[i]	2.219473e-04
@r2[i]	2.327451e-04
@r3[i]	-1.07978e-05
@r4[i]	-1.19077e-03
@r5[i]	-1.23714e-03
@r6[i]	9.688185e-04
@r7[i]	9.688185e-04
v(1)	5.179800e+00
v(2)	4.949130e+00
v(3)	4.481100e+00
v(4)	4.981968e+00
v(5)	8.811951e+00
v(6)	-1.95815e+00
v(7)	-2.94854e+00
v(8)	-1.95815e+00

Table 3: A variable preceded by @ is of type *current* and expressed in Ampere; other variables are of type *voltage* and expressed in Volt.

The results obtained through both methodologies were the same, as expected, since the circuit is straightforward and composed exclusively by linear components. As a consequence, the theoretical and the simulation models cannot differ. Were the components a bit more complex, they might have had some differences but that was not the case here.