

# Circuit Analysis - Resistances, Voltage and Current Sources

Integrated Master Engineering Physics , Técnico, University of Lisbon

Laboratory Report 1

March 23, 2021

## Contents

<b>1</b>	<b>Introduction</b>	<b>1</b>
<b>2</b>	<b>Theoretical Analysis</b>	<b>2</b>
2.1	Mesh Method . . . . .	2
2.2	Nodal Method . . . . .	2
2.3	Comparing both methods . . . . .	3
<b>3</b>	<b>Simulation Analysis</b>	<b>3</b>
<b>4</b>	<b>Conclusion</b>	<b>4</b>

## 1 Introduction

The aim of this laboratory assignment is to study a circuit composed exclusively by voltage sources ( $V_a$  and  $V_c$ ), current sources ( $I_b$  and  $I_d$ ), as well as resistors ( $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ ,  $R_5$ ,  $R_6$  and  $R_7$ ). That being said, this circuit, which is shown in the image below, contains only linear components.

It was known beforehand that:  $R_1 = 1039.3 \, \Omega$ ,  $R_2 = 2010.9 \, \Omega$ ,  $R_3 = 30411.2 \, \Omega$ ,  $R_4 = 4183.8 \, \Omega$ ,  $R_5 = 3095.8 \, \Omega$ ,  $R_6 = 2021.2 \, \Omega$ ,  $R_7 = 1022.3 \, \Omega$ ,  $V_a = 5.1798 \, V$ ,  $I_d = 0.0010044 \, A$ ,  $K_b = 0.0070875 \, A/V$  and  $K_c = 8185.8 \, V/A$ .

$N_0$  was chosen as the ground node,  $V_0 = 0 \, V$ .  $V_i$  is the voltage in node  $N_i$  and  $I_i$  ( $i = 1, 2, \dots, 7$ ) is the current that goes through mesh  $i$  counterclockwise ( $i = A, B, C, D$ ).

In Section 2, a theoretical analysis of the circuit is presented following two of the most common methods: the mesh method and the nodal method (in the former the objective was to find the values of the current in each essential mesh, whereas in the latter it was to find the potential in each node). In Section 3, the circuit is analysed by simulation. Finally, the comparison between both types of analysis and the conclusions of this study are in Section 4.

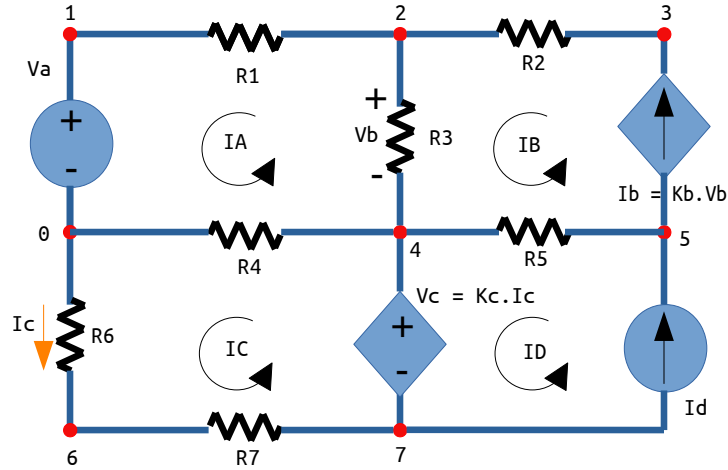


Figure 1: The circuit in study

## 2 Theoretical Analysis

### 2.1 Mesh Method

In the mesh method, equations are written for essential meshes, using Kirchhoff's voltage law (KVL), which states that "the directed sum of the potential differences (voltages) around any closed loop is zero". There are also additional equations.

In this method, as well as in the next one, Ohm's Law,  $V = RI \Leftrightarrow I = \frac{V}{R}$ , was used several times.

$$\begin{cases} R_6 I_3 + R_7 I_3 - V_c + R_4 (I_3 - I_1) = 0 & (1) \\ V_a - R_4 (I_3 - I_1) - V_b + R_1 I_1 = 0 & (2) \\ V_c = K_c I_c & (3) \\ I_b = K_b V_b & (4) \\ I_3 = I_c & (5) \\ I_4 = I_d & (6) \\ I_2 = I_b & (7) \\ (I_2 - I_1) R_3 = V_b & (8) \end{cases} \quad (1)$$

KVL was used for meshes *C* and *A* in equations (1) and (2) respectively. As for equations (3) and (4), they were based on the information given for voltage source  $V_c$  and current source  $I_b$ . Equations (5), (6) and (7) were by inspection meshes *C* and *D*. Lastly, in equation (8) it was known that the difference of potential between the terminals of resistor  $R_3$  was  $V_b$ , but because of Ohm's law it is also equal to  $(I_2 - I_1)R_3$ ,  $(I_2 - I_1)$  being the current that goes through that same resistor.

### 2.2 Nodal Method

In the nodal method, a set of equation is written based on Kirchhoff's current law (KCL), according to which "the algebraic sum of currents in a network of conductors meeting at a point is zero", which means that the sum of currents flowing into that node is equal to the sum of currents flowing out of that node. Plus, there are some additional equations.

Name	Value [A or V]
$I_A$	-0.000222
$I_B$	-0.000233
$I_C$	0.000969
$I_D$	0.001004

Table 1: Operating point. A variable preceded by @ is of type *current* and expressed in Ampere; other variables are of type *voltage* and expressed in Volt.

$$\begin{cases}
 V_0 = 0 & (1) \\
 V_1 - V_0 = V_a & (2) \\
 \frac{V_2 - V_1}{R_1} + \frac{V_2 - V_4}{R_3} + \frac{V_3 - V_2}{R_2} = 0 & (3) \\
 \frac{V_3 - V_2}{R_2} - (V_2 - V_4)K_b = 0 & (4) \\
 \frac{V_0 - V_6}{R_6} - \frac{V_6 - V_7}{R_7} = 0 & (5) \\
 \frac{V_5 - V_4}{R_5} + K_b(V_2 - V_4) - I_d = 0 & (6) \\
 V_4 - V_7 = K_c \frac{V_0 - V_6}{R_6} & (7) \\
 \frac{V_2 - V_4}{R_3} + \frac{V_5 - V_4}{R_5} + \frac{V_6 - V_7}{R_7} - \frac{V_4 - V_0}{R_4} - I_d = 0 & (8)
 \end{cases} \quad (2)$$

Equation (1) refers to  $N_0$  being the ground node and equation (2) is reached by inspection in voltage source  $V_a$ . In equations (3), (4), (5) and (6) we have KCL for nodes  $N_2$ ,  $N_3$ ,  $N_6$  and  $N_5$ , respectively. Using Ohm's law, one knows that  $\frac{V_2 - V_1}{R_1}$  is the current that goes through resistor  $R_1$ ,  $\frac{V_3 - V_2}{R_2}$  the one that goes through  $R_2$ ,  $\frac{V_2 - V_4}{R_3}$  through  $R_3$ ,  $\frac{V_5 - V_4}{R_5}$  through  $R_5$ ,  $\frac{V_0 - V_6}{R_6}$  through  $R_6$ ,  $\frac{V_6 - V_7}{R_7}$  through  $R_7$ .

Name	Value [A or V]
$V_0$	0.000000
$V_1$	5.179800
$V_2$	4.949130
$V_3$	4.481100
$V_4$	4.981968
$V_5$	8.811951
$V_6$	-1.958148
$V_7$	-2.948538

Table 2: Operating point. A variable preceded by @ is of type *current* and expressed in Ampere; other variables are of type *voltage* and expressed in Volt.

**maybe explaining these equations a little better??**

### 2.3 Comparing both methods

After solving a linear system of equations with Octave, it was found out that.

## 3 Simulation Analysis

The aforementioned circuit was simulated using the ngspice simulator, which returned the following values:

Name	Value [A or V]
@gb[i]	-2.32745e-04
@id[current]	1.004395e-03
@r1[i]	2.219473e-04
@r2[i]	2.327451e-04
@r3[i]	-1.07978e-05
@r4[i]	-1.19077e-03
@r5[i]	-1.23714e-03
@r6[i]	9.688185e-04
@r7[i]	9.688185e-04
v(1)	5.179800e+00
v(2)	4.949130e+00
v(3)	4.481100e+00
v(4)	4.981968e+00
v(5)	8.811951e+00
v(6)	-1.95815e+00
v(7)	-2.94854e+00
v(8)	-1.95815e+00

Table 3: A variable preceded by @ is of type *current* and expressed in Ampere; other variables are of type *voltage* and expressed in Volt.

## 4 Conclusion

In the end, one can say that the objectives defined for this laboratory session were met. Through the theoretical analysis, all node potentials and mesh currents were determined, with the results proving to be consistent and coherent. Meanwhile, the circuit simulation returned values for the node potentials and some branch currents, all of which matched those determined previously. This was to be expected as the circuit is very straightforward, being composed entirely of time-invariant linear components.